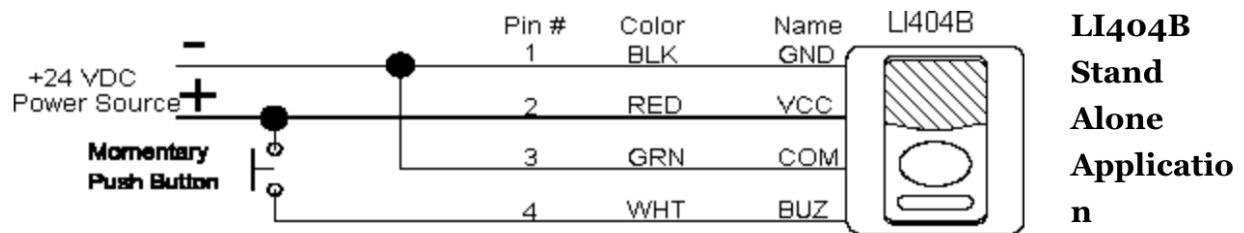


Tek-ENTRY TekTip: Current Capability LI404B with +24VDC power source

Recently, we have received several technical support calls requesting help for this application.

The +24VDC power source, indicated on the wiring diagram, will need a 250ma minimum of current capability. For each additional strobe unit to be activated simultaneously, increase the supply's current capability by 200ma.



(Aug. 1995)